

RISC PLA/FSM Lab – MIPS

Description:

In this lab, we were asked to design an FSM controller for a MIPS process with more than six RISC instructions. We also needed to include control signals for the states and Boolean equations, state equations, and a PLA.

Equipment Used:

- MS Paint

Procedure:

I started by drawing the FSM in MS Paint, following the lectures located in the Week 11 folder. Then I noted the control signals for each state, which I used to create the state equations. After that, I created a truth table for the NS bits and wrote down the Boolean equations for all the variables. Finally, I utilized all this information to create a PLA diagram in MS paint.

Results:

Control Signals for Each State

- State 0:
 - MemRead
 - $ALUSrcA = 0$
 - $IorD = 0$
 - IRWrite
 - $ALUSrcB = 01$
 - $ALUOp = 00$

- PCWrite
 - PCSrc = 00
- State 1:
 - ALUSrcA = 0
 - ALUSrcB = 11
 - ALUOp = 00
- State 2:
 - ALUSrcA = 1
 - ALUSrcB = 10
 - ALUOp = 00
- State 3:
 - MemRead
 - IorD = 1
- State 4:
 - RegDst=0
 - RegWrite
 - MemtoReg=1
- State 5:
 - MemWrite
 - IorD = 1
- State 6:
 - ALUSrcA = 1
 - ALUSrcB = 00

- $ALUOp = 10$
- State 7:
 - $RegDst = 1$
 - $RegWrite$
 - $MemtoReg = 0$
- State 8:
 - $ALUSrcA = 1$
 - $ALUSrcB = 00$
 - $ALUOp = 01$
 - $PCWriteCond$
 - $PCSource = 01$
- State 9:
 - $PCWrite$
 - $PCSource = 10$

Control Signals to Boolean Equations:

- $PCWrite = state0 + state9$
- $PCWriteCond = state8$
- $PCSource1 = state9$
- $PCSource0 = state8$
- $IorD = state3 + state5$
- $MemRead = state0 + state3$
- $MemWrite = state5$
- $MemToReg = state4$

- $ALUOp1 = state6$
- $ALUOp0 = state8$
- $ALUSrcA = state2 + state6 + state8$
- $ALUSrcB1 = state1 + state2$
- $ALUSrcB0 = state0 + state1$
- $RegWrite = state4 + state7$
- $RegDst = state7$
- $IRWrite = state0$

State Equations:

- $Next\ State\ 0 = state4 + state5 + state7 + state8 + state9$
- $Next\ State\ 1 = state0$
- $Next\ State\ 2 = state1(lw + sw)$
- $Next\ State\ 3 = state2(lw)$
- $Next\ State\ 4 = state3$
- $Next\ State\ 5 = state2(sw)$
- $Next\ State\ 6 = state1(R-type)$
- $Next\ State\ 7 = state6$
- $Next\ State\ 8 = state1(beq)$
- $Next\ State\ 9 = state1(jump)$
- $NS0 = Next\ State\ 1 + Next\ State\ 3 + Next\ State\ 5 + Next\ State\ 7 + Next\ State\ 9 = state0$
 $+ state2(lw) + state2(sw) + state6 + state1(jump)$

- $NS1 = \text{Next State 2} + \text{Next State 3} + \text{Next State 6} + \text{Next State 7} = \text{state1(lw+sw)} + \text{state2(lw)} + \text{state1(R-type)} + \text{state6}$
- $NS2 = \text{Next State 4} + \text{Next State 5} + \text{Next State 6} + \text{Next State 7} = \text{state3} + \text{state2(sw)} + \text{state1(R-type)} + \text{state6}$
- $NS3 = \text{Next State 8} + \text{Next State 9} = \text{state1(beq)} + \text{state1(jump)}$

Table 1 A truth table for the NS bits.

NS3	NS2	NS1	NS0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

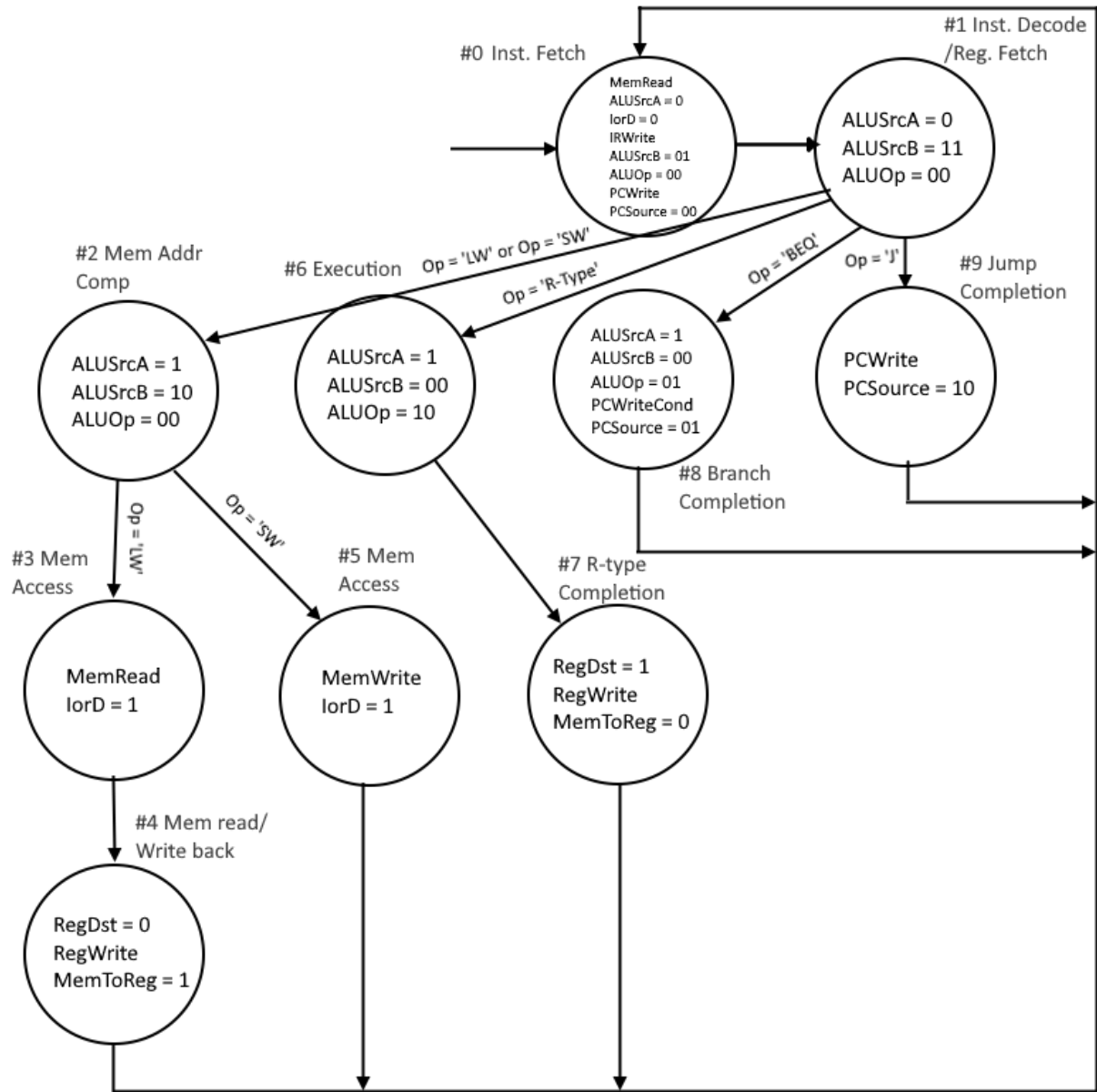


Figure 1 An FSM controller for the MIPS processor.

 


Figure 2 A PLA diagram for the MIPS processor.

Conclusions:

This lab helped me understand the process of designing an FSM and PLA for a processor datapath. Although it looked intimidating at first, I realized that it's actually relatively simple. This knowledge will help me in the future when I have to add additional instructions to a datapath.